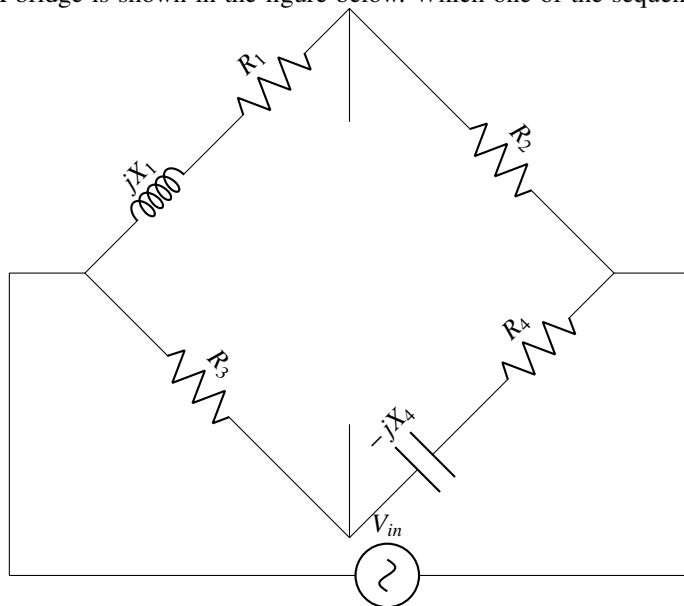


# 2007-EE

EE24BTECH11008-ASLIN GARVASIS

- 69) Which one of the following statements regarding the INT (interrupt) and the BRQ (bus request) pins in a CPU is true ?
- The BRQ pin is sampled after every instruction cycle, but the INT is sampled after every machine cycle
  - Both INT and BRQ are sampled after every machine cycle
  - The INT pin is sampled after every instruction cycle, but the BRQ is sampled after every machine cycle
  - Both INT and BRQ are sampled after every instruction cycle
- 70) A bridge is shown in the figure below. Which one of the sequences given below is most suitable for balancing the bridge



?

- First adjust  $R_4$  and then adjust  $R_1$
- First adjust  $R_2$  and then adjust  $R_3$
- First adjust  $R_2$  and then adjust  $R_4$
- First adjust  $R_4$  and then adjust  $R_2$

## Common Data Questions


**Common Data for Questions 71, 72, 73 :**

A three phase squirrel cage induction motor has a starting current of seven times the full load current and full load slip of 5%

- 71) If an autotransformer is used for reduced voltage starting to provide 1.5 per unit starting torque, the transformer ratio (%) should be
- 57.77%
  - 72.56%
  - 78.25%
  - 81.33%
- 72) If a star-delta starter is used to start this induction motor, the per unit starting torque will be
- 0.607
  - 0.816
  - 1.225
  - 1.616
- 73) If a starting torque of 0.5 per unit is required then the per unit starting current should be
- 4.65
  - 3.75
  - 3.16
  - 2.13

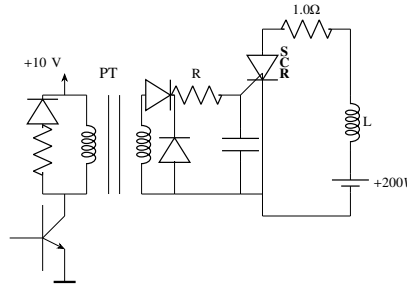**Common Data for Questions 74, 75 :**

A : 1 Pulse Transformer (PT) is used to trigger the SCR in the adjacent figure. The SCR is rated at  $1.5(kV)$ ,  $250(A)$  with  $I_L = 250(mA)$ ,  $I_H = 150(mA)$ , and  $I_{Gmax} = 150$ ,  $I_{Gmin} = 100(mA)$ . The SCR is connected to an inductive load, where  $L=150(mH)$  in series with a small resistance and the supply voltage is  $200(V)$  dc. The forward drops of all transistors/diodes during ON state are  $1.0(0V)$ .



74) The resistor R should be

- a)  $4.4(k\Omega)$
- b)  $470(\Omega)$
- c)  $47(\Omega)$
- d)  $4.7(\Omega)$

75) The minimum approximate volt-second rating of the pulse transformer suitable for triggering the SCR should be; (volt-second rating is t

- a)  $2000(\mu V - s)$
- b)  $200(\mu V - s)$
- c)  $20(\mu V - s)$
- d)  $2.0(\mu V - s)$

**Linked Answer Questions: Q.76 to Q.85 carry two marks each.**

**Statement for Linked Answer Questions 76&77 :**

An inductor designed with 400 turns coil wound on an iron core of  $16(cm^2)$  cross sectional area with a cut of an air gap length of  $1(mm)$ . The coil is connected to a  $230(V)$ ,  $5050(Hz)$  ac supply. Neglect coil resistance, core loss, iron reluctance and leakage inductance. ( $\mu_0 = 4\pi \times 10^{-7} H/m$ )

76) The current in the inductor is

- a)  $18.08(A)$
- b)  $9.04(A)$
- c)  $4.56(A)$
- d)  $2.28(A)$

77) The average force on the core to reduce the air gap will be

- a)  $832.29(N)$
- b)  $1666.22(N)$
- c)  $3332.47(N)$
- d)  $6664.84(N)$

**Statement for Linked Answer Questions 78&79;**

Cayley-Hamilton Theorem states that a square matrix satisfies its own characteristic equation. Consider a matrix

$$A = \begin{pmatrix} -3 & 2 \\ -1 & 0 \end{pmatrix}$$

78) A satisfies the relation

- a)  $A + 3I + 2A^{-1} = 0$
- b)  $A + 2I + 2A = 0$
- c)  $(A + I)(A + 2I) = 0$
- d)  $\exp(A)$


79)  $A^9$  equals

- a)  $511A + 310I$

- b)  $309A + 104I$
- c)  $154A + 155I$
- d)  $\exp(9A)$

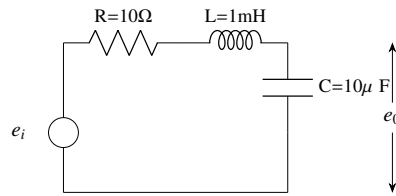**Statement for Linked Answer Questions 80&81:**

Consider the R-L-C circuit shown in figure



- 80) For a step-input  $e_i$  the overshoot in the output  $e_o$  will be
- a) 0, since the system is not under-damped
  - b) 5%
  - c) 16%
  - d) 48%
- 81) If the above step response is to be observed on a non-storage CRO, then it would be best to have the  $e_i$  as a
- a) step function
  - b) square wave of frequency 50 (Hz)
  - c) square wave of frequency 300 (Hz)
  - d) square wave of frequency 2.0 (kHz)

**Statement for Linked Answer Questions 82&83 :**

The associated figure shows the two types of rotate right instructions  $R1$ ,  $R2$  available in a microscope where Reg is a 8– bit register and C is the carry bit. The rotate left instructions  $L1$  and  $L2$  are similar except that C now links the most significant Reg instead of the least significant one.



- 82) Suppose Reg contains the 2's complement number 111010110. If this number is divided by 2 the answer should be
- a) 01101011
  - b) 10010101
  - c) 11101001
  - d) 11101011
- 83) Such a division can be correctly performed by the following set of operations
- a)  $L2, R2, R1$
  - b)  $L2, R1, R2$
  - c)  $R2, L1, R2$
  - d)  $R1, L2, R2$

**Statement Linked Answer Questions 84&85 :**

- 84) A signal is processed by a casual filter with transfer function  $G(s)$ . For a distortion free output signal waveform,  $G(s)$  must
- a) provide zero phase shift for all frequency
  - b) provide constant phase shift for all frequency
  - c) provide linear phase shift that is proportional to frequency
  - d) provide a phase shift that is inversely proportional to frequency
- 85)  $G(z) = \alpha z^{-1} + \beta z^{-3}$  is a low-pass digital filter with a phase characteristics same as that of the above question if
- a)  $\alpha = \beta$
  - b)  $\alpha = -\beta$
  - c)  $\alpha = \beta^{(\frac{1}{3})}$
  - d)  $\alpha = \beta^{(\frac{-1}{3})}$